

Last Time

- Transient response when connecting a circuit
- How long until steady state is reached?
- Introduction to Resistors
- Energy conservation in a circuit
- Kirchhoff's Voltage Loop Law
- Batteries

Today




CAPACITORS.
Lots of Capacitors.



Connecting a Circuit

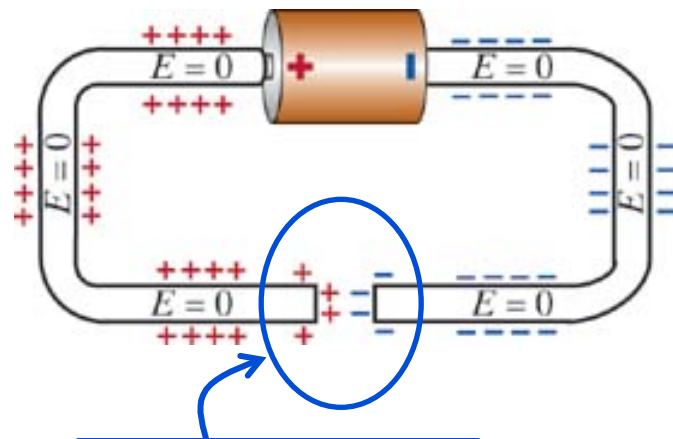*What happens just before
a circuit is connected?*



Think about
the gap...

Before the circuit is connected:

- No current flows $I = |q|nAu|\vec{E}| = 0$
- System is in **equilibrium**:


$$\vec{E} = 0$$

$$\bar{v} = u|\vec{E}| = 0$$


- Charge on faces of gap

Building a Capacitor


Add plates at the gap

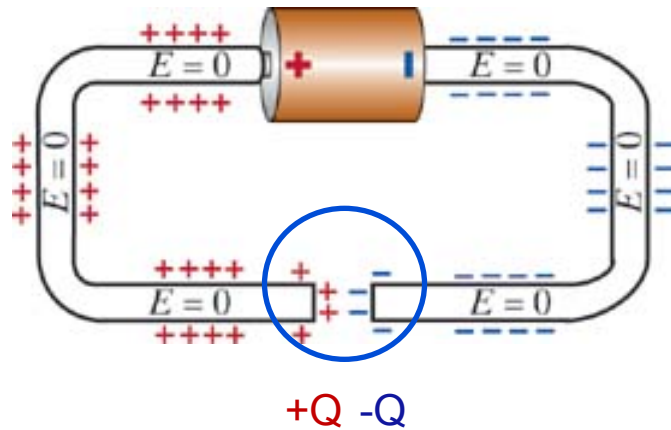

Gap Charge


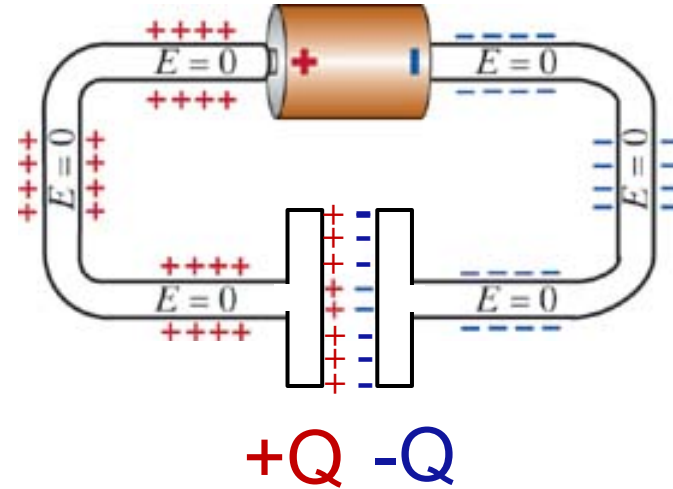


Bigger Gap Charge


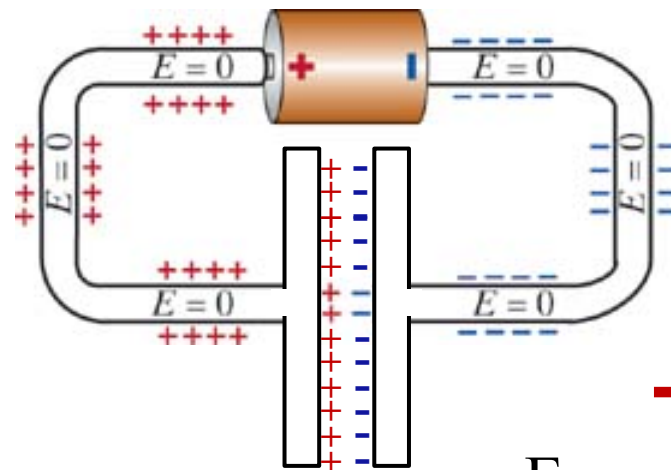


Even Bigger Gap Charge


Capacitor: Construction and Symbols

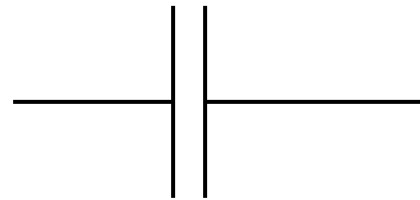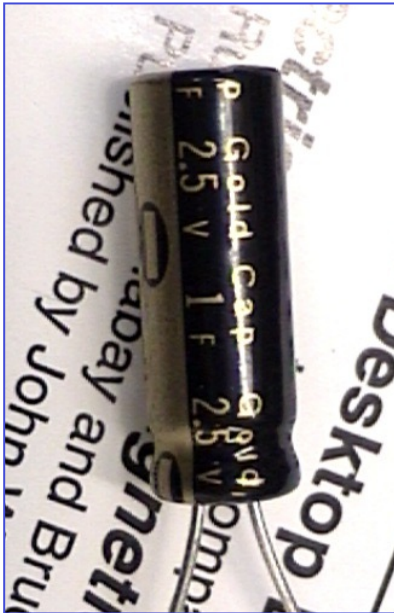

Circuit Symbol

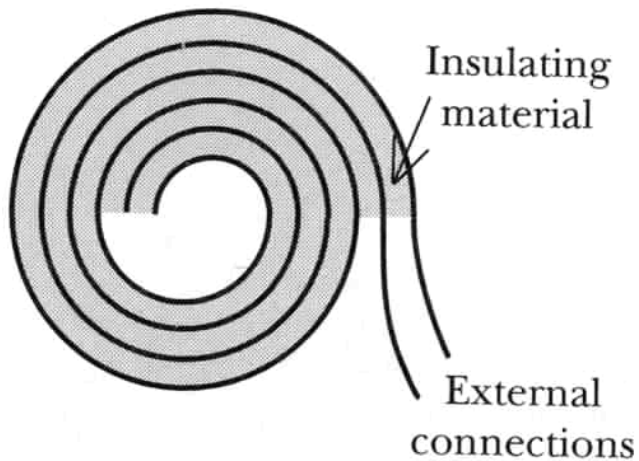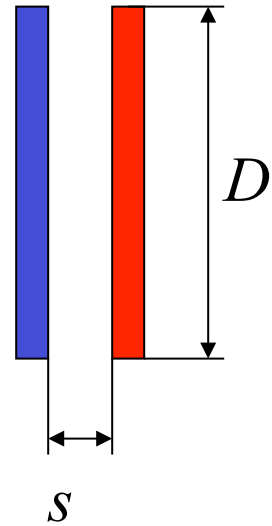





Capacitor: Charging

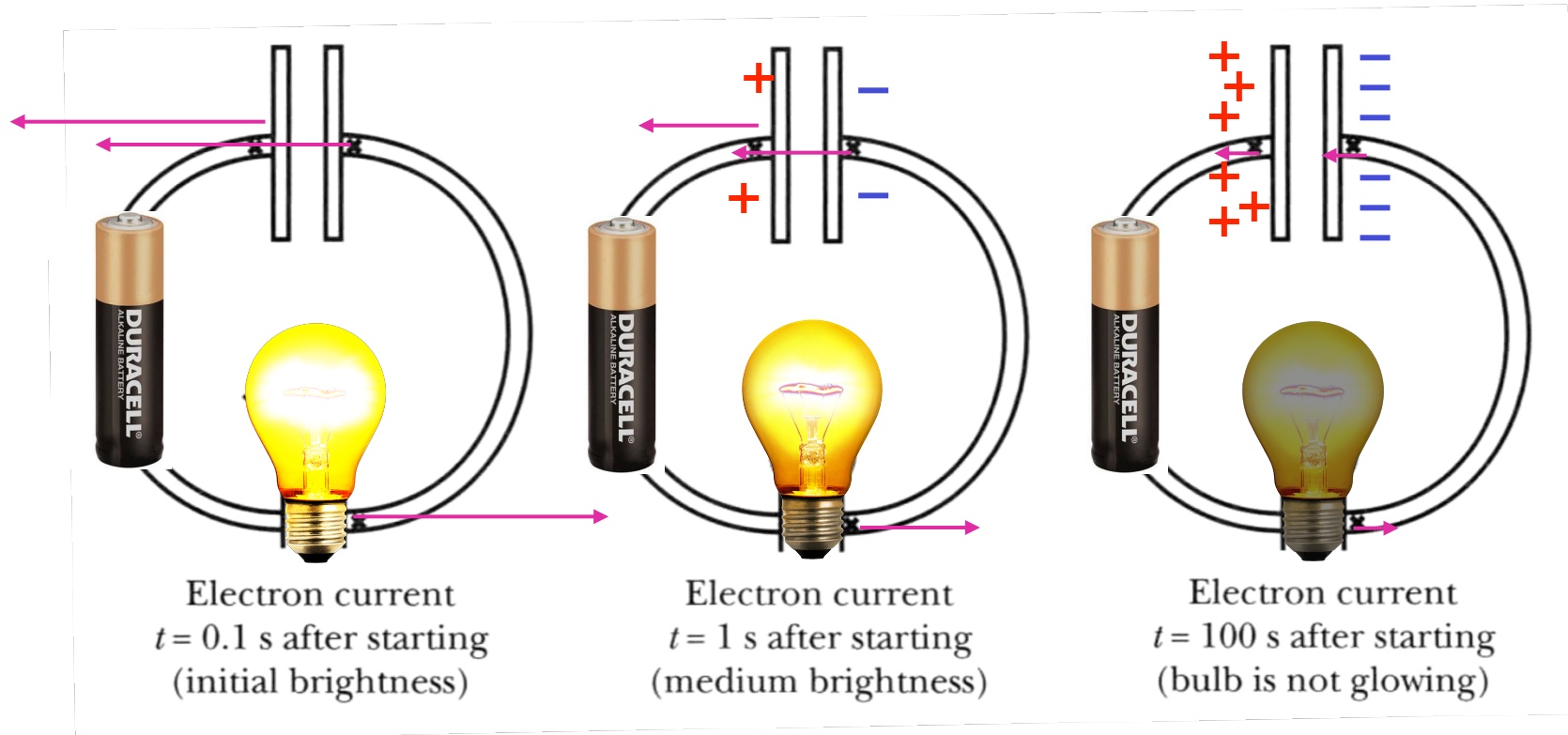

Current flows into & out of capacitor, but not through it.
Charges build up on capacitor until current finally stops. (~ 10 sec)

Fringe field of a capacitor rises until $E=0$ in a wire – static equilibrium.

Charging Capacitor

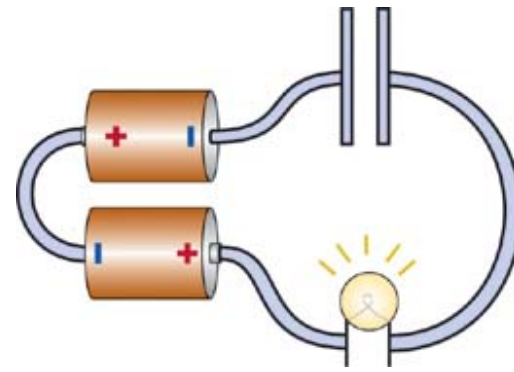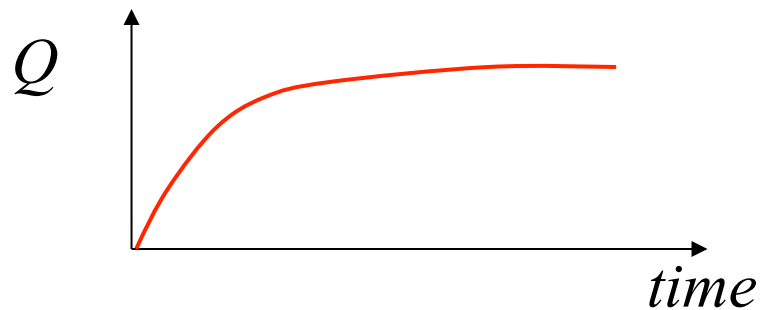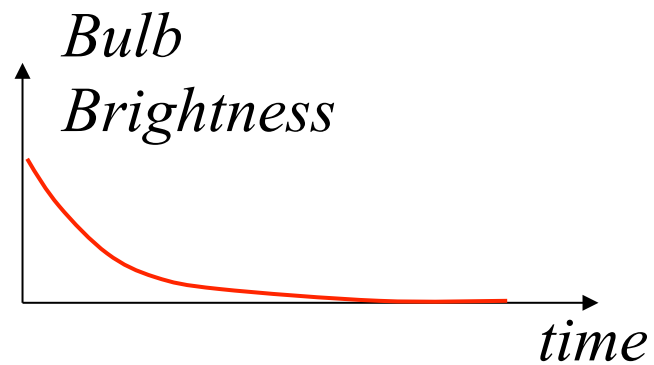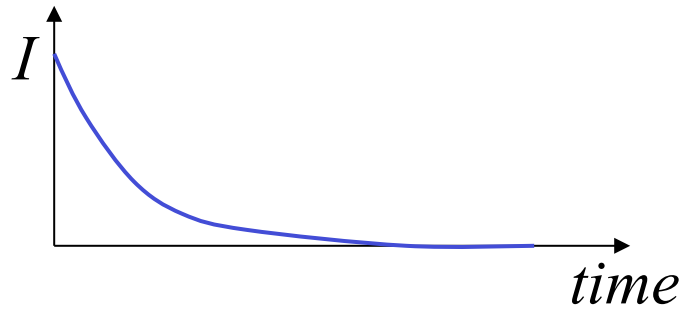



Capacitor: Charging

Why does current ultimately stop flowing in the circuit?

Ultimately, the fringe field of the capacitor and the field due to charges on the wire are such that $E=0$ inside the wire. At this point, $i=0$.

Capacitor: Discharge








Start with a charged capacitor

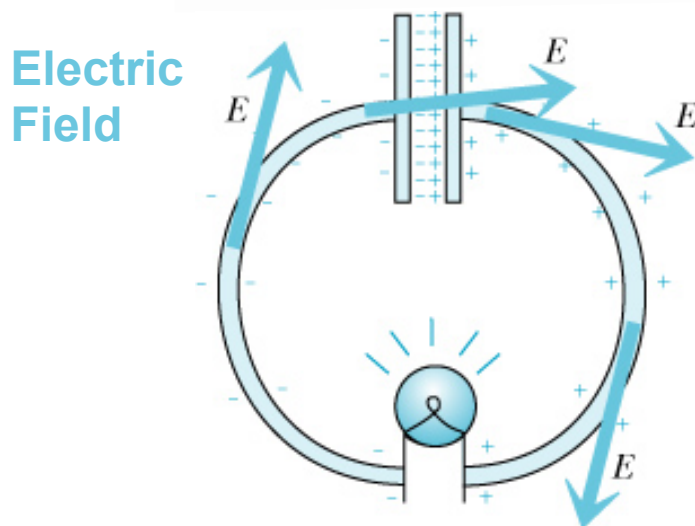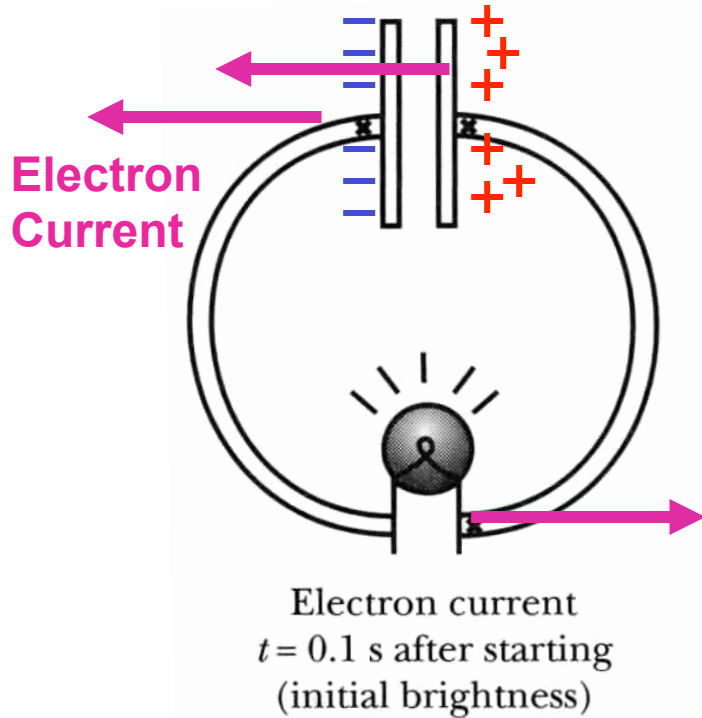


Charging

"One of these things
is not like other"

Discharging

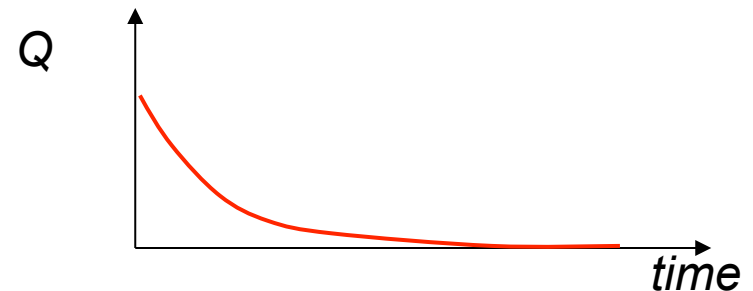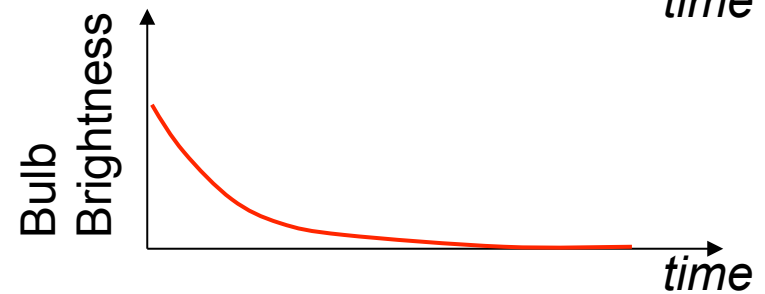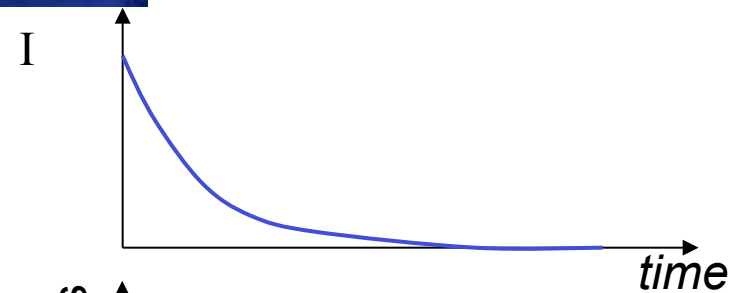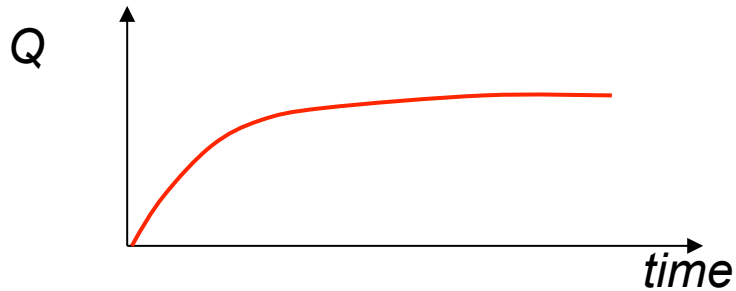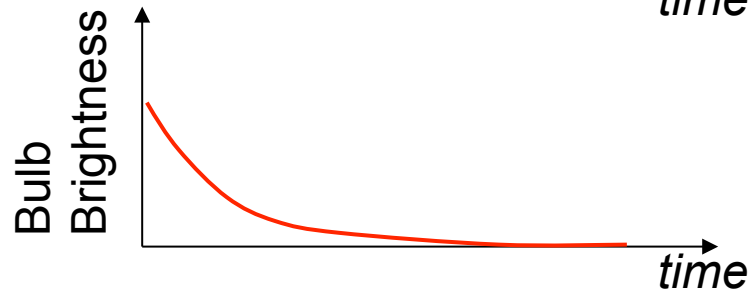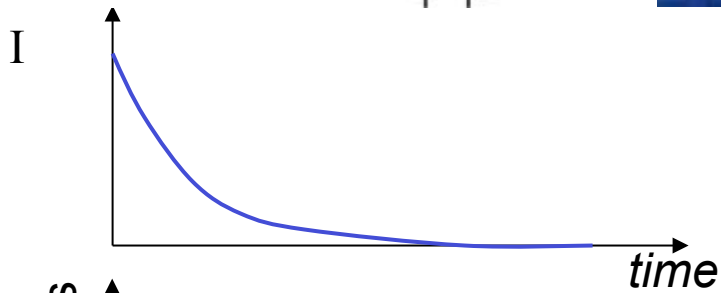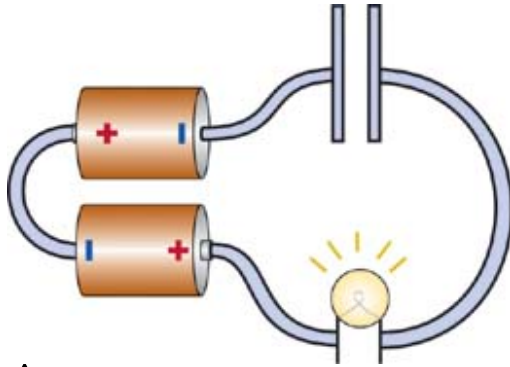

How is Discharging Possible?

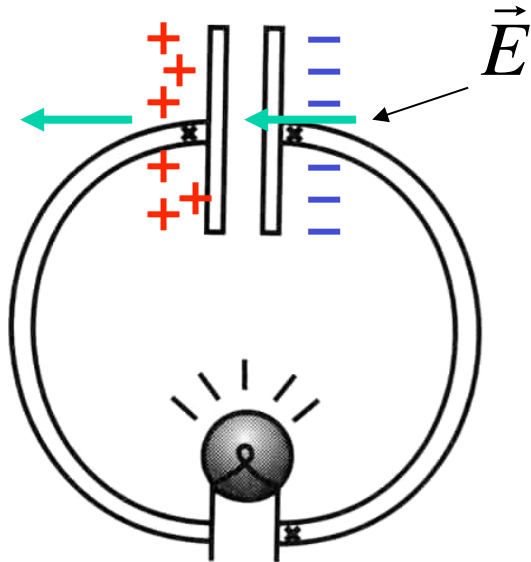



Positive and negative charges are attracted to each other: how can they leave the plates?

Two ways to think about it:

Opposites attract, but the like charges are repelling more

Fringe field is not zero

The Effect of Different Light Bulbs

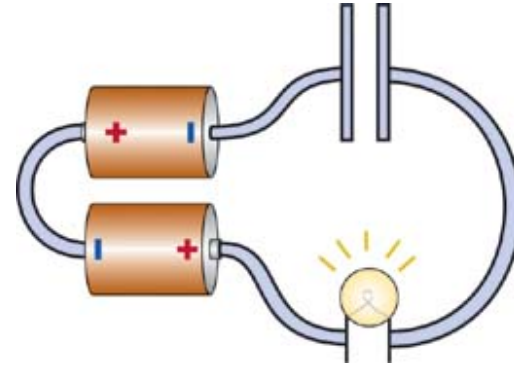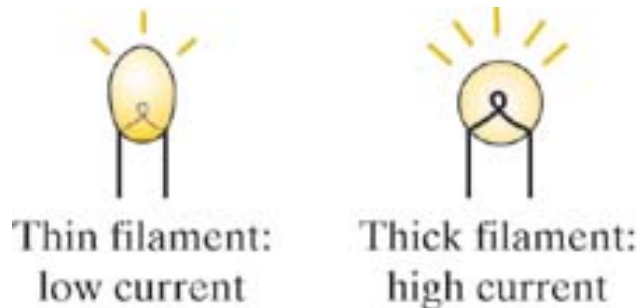

Which light bulb will glow longer?

- 1) Thick filament is brighter → capacitor gets charged more?
- 2) Thin filament glows longer → capacitor gets charged more?

In equilibrium:


Voltage across capacitor = Voltage across battery

Capacitor charged by same amount in both cases.

Definition of “Capacitance”

$$Q = C|\Delta V|$$

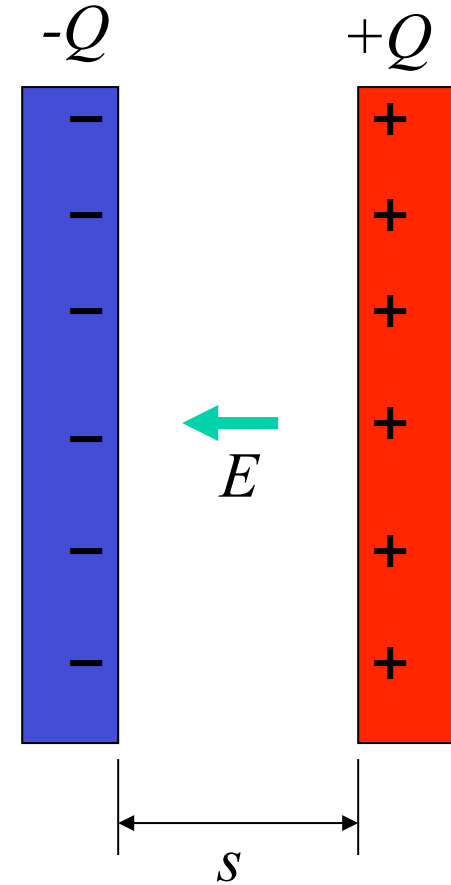Mnemonic Device:
“Quacks are CoVered”
(by medical insurance)



Capacitance


$$Q = C|\Delta V|$$

Electric field in a capacitor:

$$E = \frac{Q/A}{\epsilon_0}$$

$$\Delta V = -\int_i^f \vec{E} \cdot d\vec{l} \longrightarrow |\Delta V| = Es$$

$$|\Delta V| = \frac{Q/A}{\epsilon_0} s \longrightarrow Q = \frac{\epsilon_0 A}{s} |\Delta V|$$

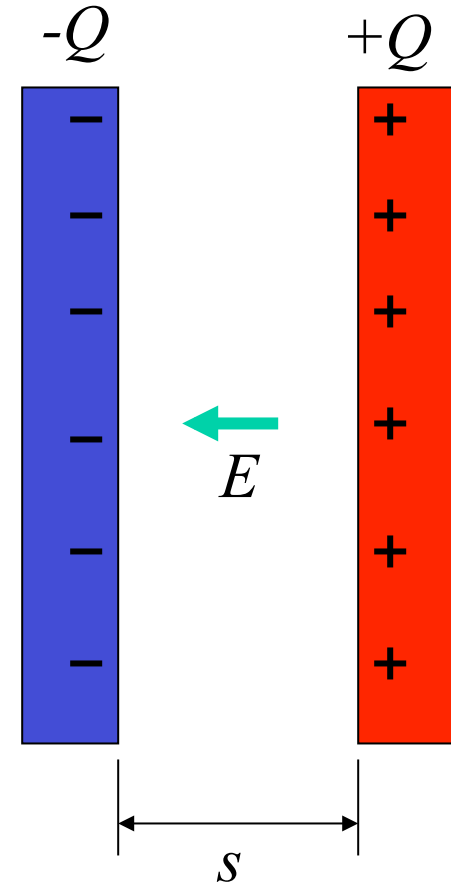


Capacitance of a parallel-plate capacitor:

$$C = \frac{\epsilon_0 A}{s}$$


iClicker

Effect of the Capacitor Disk Size

$$Q = \frac{\epsilon_0 A}{s} |\Delta V|$$

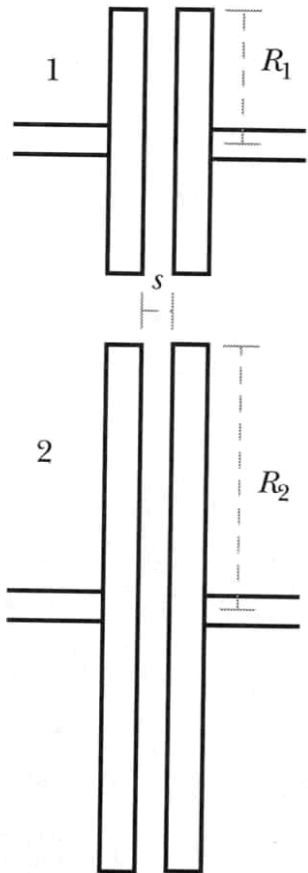

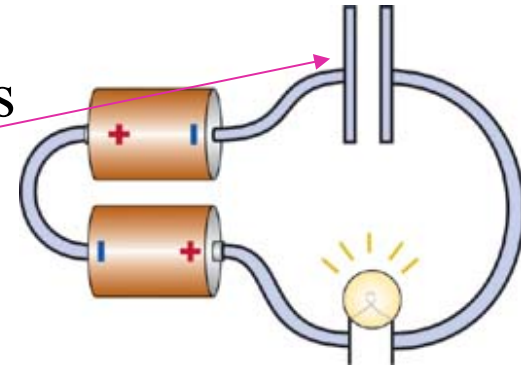Use two different capacitors
in the same circuit





After charging, which capacitor holds more charge?

Charge the capacitor, then delete the batteries:
Which capacitor runs the bulb longer?

Effect of the Capacitor Disk Separation


$$Q = \frac{\epsilon_0 A}{s} |\Delta V|$$

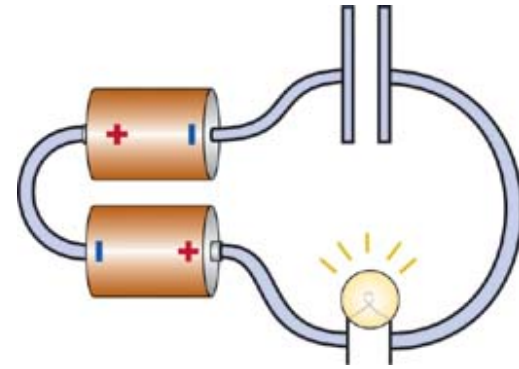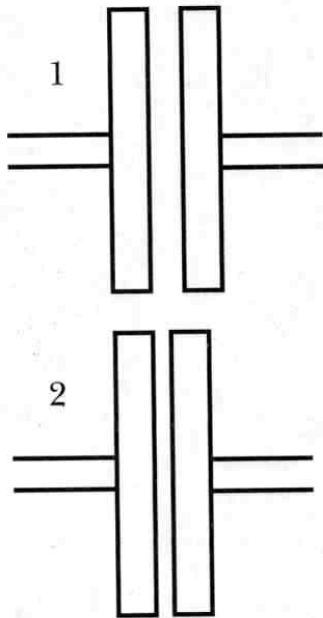

After charging, which capacitor holds more charge?

Charge the capacitor, then delete the batteries:
Which capacitor runs the bulb longer?

Parallel Capacitors

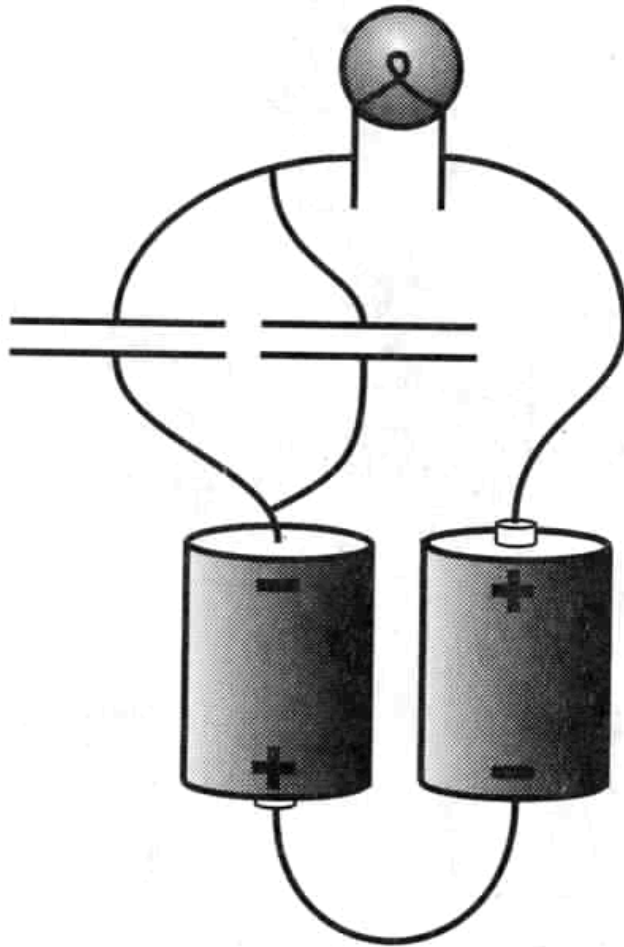


Initial moment: brighter?

Fringe field: $E_1 \approx \frac{Q/A}{2\epsilon_0} \frac{s}{R}$

Capacitors in parallel effectively increase A


A Seemingly Isolated Light Bulb

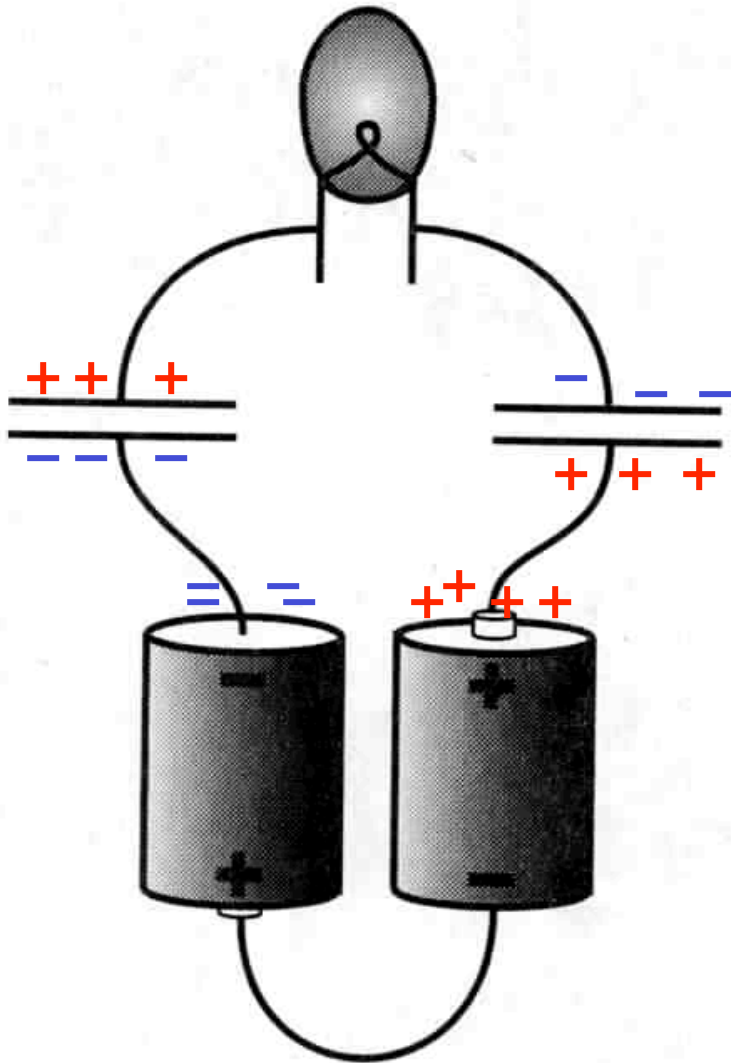

Will it glow at all?

How do electrons flow through the bulb?

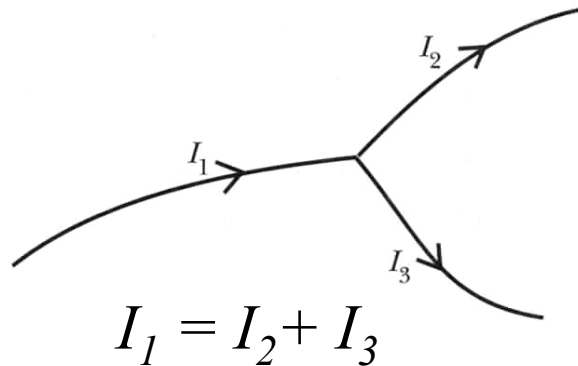
The Current Node Rule in a Capacitor Circuit



Charge conservation:

$$\sum_i I_i = 0 \quad \begin{array}{l} I_i > 0 \text{ for incoming} \\ I_i < 0 \text{ for outgoing} \end{array}$$

...in steady state

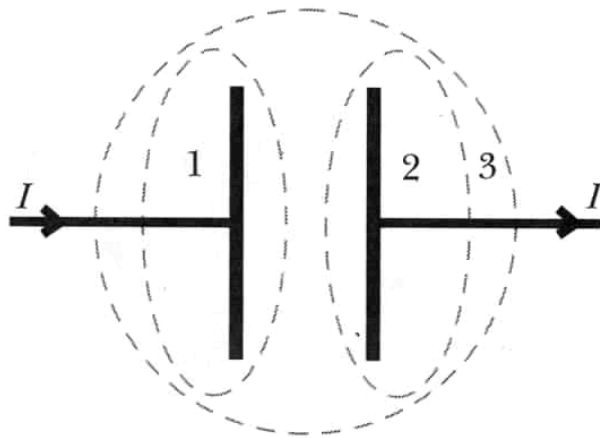

Capacitor transients:

not a steady state!

Cannot use Kirchhoff rule for a part of a capacitor (area 1 or 2)

But can use for capacitor as a whole (area 3)

A Capacitor With an Insulator Between the Plates

No insulator:

$$E = \frac{Q/A}{\epsilon_0}$$

$$|\Delta V| = Es$$

$$|\Delta V| = \frac{Q/A}{\epsilon_0} s$$

$$Q = \left(\frac{\epsilon_0 A}{s} \right) |\Delta V|$$

$$C = \frac{\epsilon_0 A}{s}$$

With insulator:


$$E = \frac{Q/A}{K\epsilon_0}$$

$$|\Delta V| = Es$$

$$|\Delta V| = \frac{Q/A}{K\epsilon_0} s$$

$$Q = \left(\frac{K\epsilon_0 A}{s} \right) |\Delta V|$$

$$C = K \frac{\epsilon_0 A}{s}$$

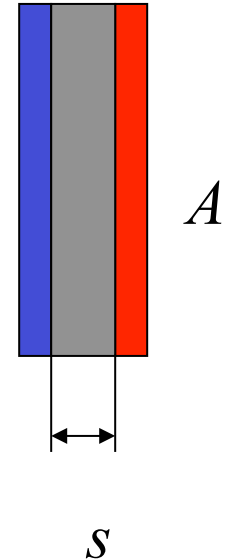

Today



CAPACITORS.
Lots of Capacitors.

